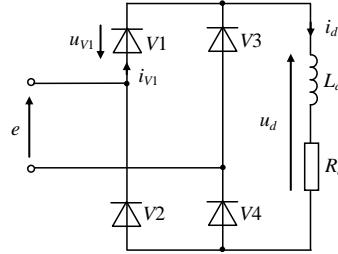


## Single-phase bridge rectifier with inductive load

$$e = 326 \sin 100\pi t, \text{ V}$$

$$L_d = 1 \text{ H}$$

$$R_d = 1 \Omega$$



### Analysis

$$\omega = 100\pi \text{ rad/s}$$

$$f = \frac{\omega}{2\pi}$$

$$f = 50 \text{ Hz}$$

$$T = \frac{1}{f}$$

$$T = 20 \text{ ms}$$

$$\tau = \frac{L_d}{R_d}$$

$$\tau = 1 \text{ s}$$

$$\tau \gg \frac{T}{2} \Rightarrow i_d \approx \text{const.} = I_d(0)$$

$$U_d(0) = \frac{2}{\pi} \hat{E}$$

$$U_d(0) = 207,5 \text{ V}$$

$$U_d(0) = U_{Ld}(0) + U_{Rd}(0)$$

$$U_{Ld}(0) = 0$$

$$U_d(0) = U_{Rd}(0)$$

$$I_d(0) = \frac{U_d(0)}{R_d}$$

$$I_d(0) = 207,5 \text{ A}$$

$$I_{V1}(0) = I_{V2}(0) = I_{V3}(0) = I_{V4}(0) = \frac{I_d(0)}{2}$$

$$I_{V1}(0) = 103,8 \text{ A}$$


$$I_{V1} = I_{V2} = I_{V3} = I_{V4} = I_d(0) \frac{1}{\sqrt{2}}$$

$$I_{V1} = 146,8 \text{ A}$$


Waveforms obtained by changing of parameters  $R_d$  and  $L_d$  will be presented.

The waveforms are simulated in Simplorer 6.0.
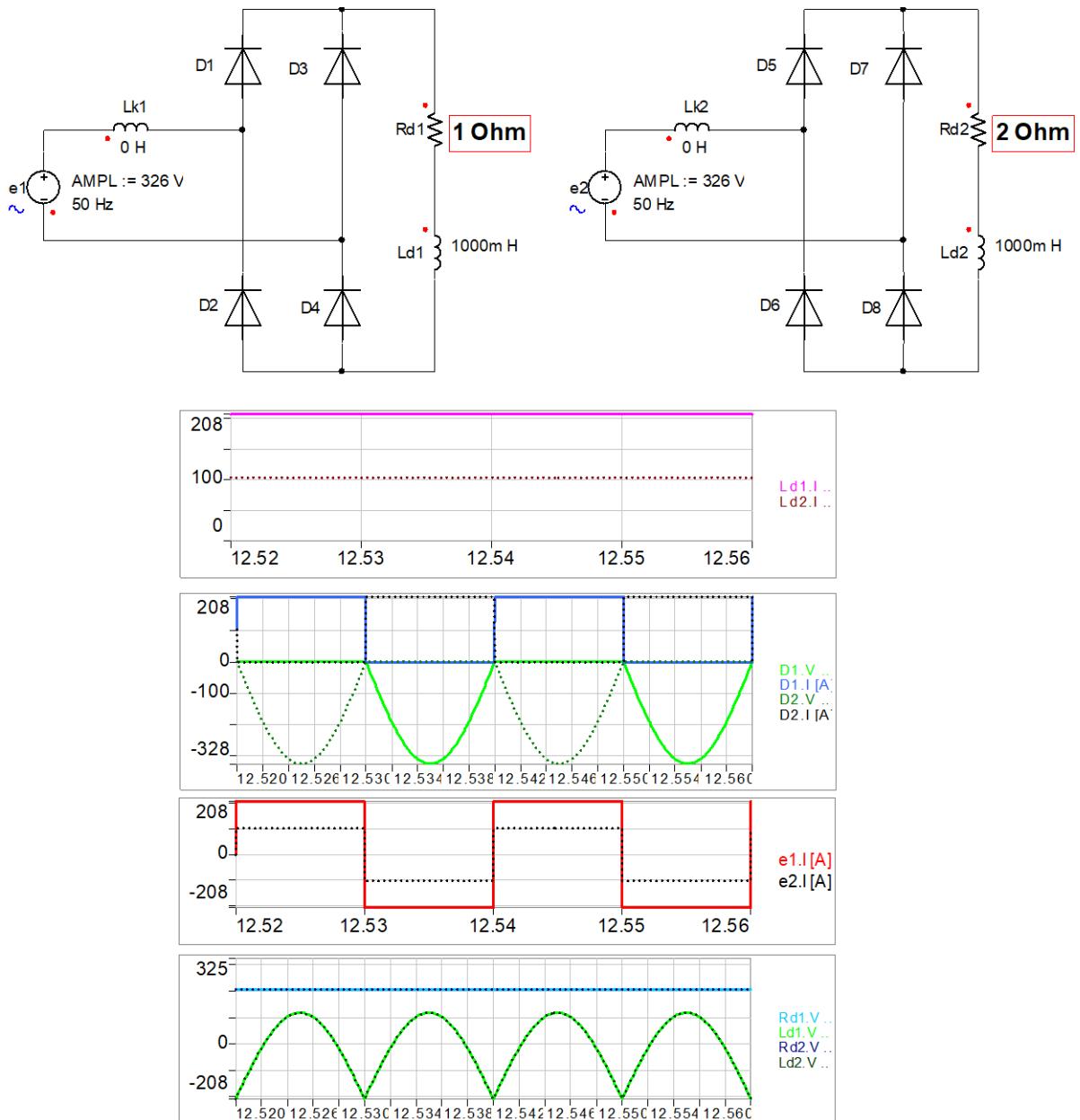
## Dependance of the rectifier waveforms on the load resistance $R_d$


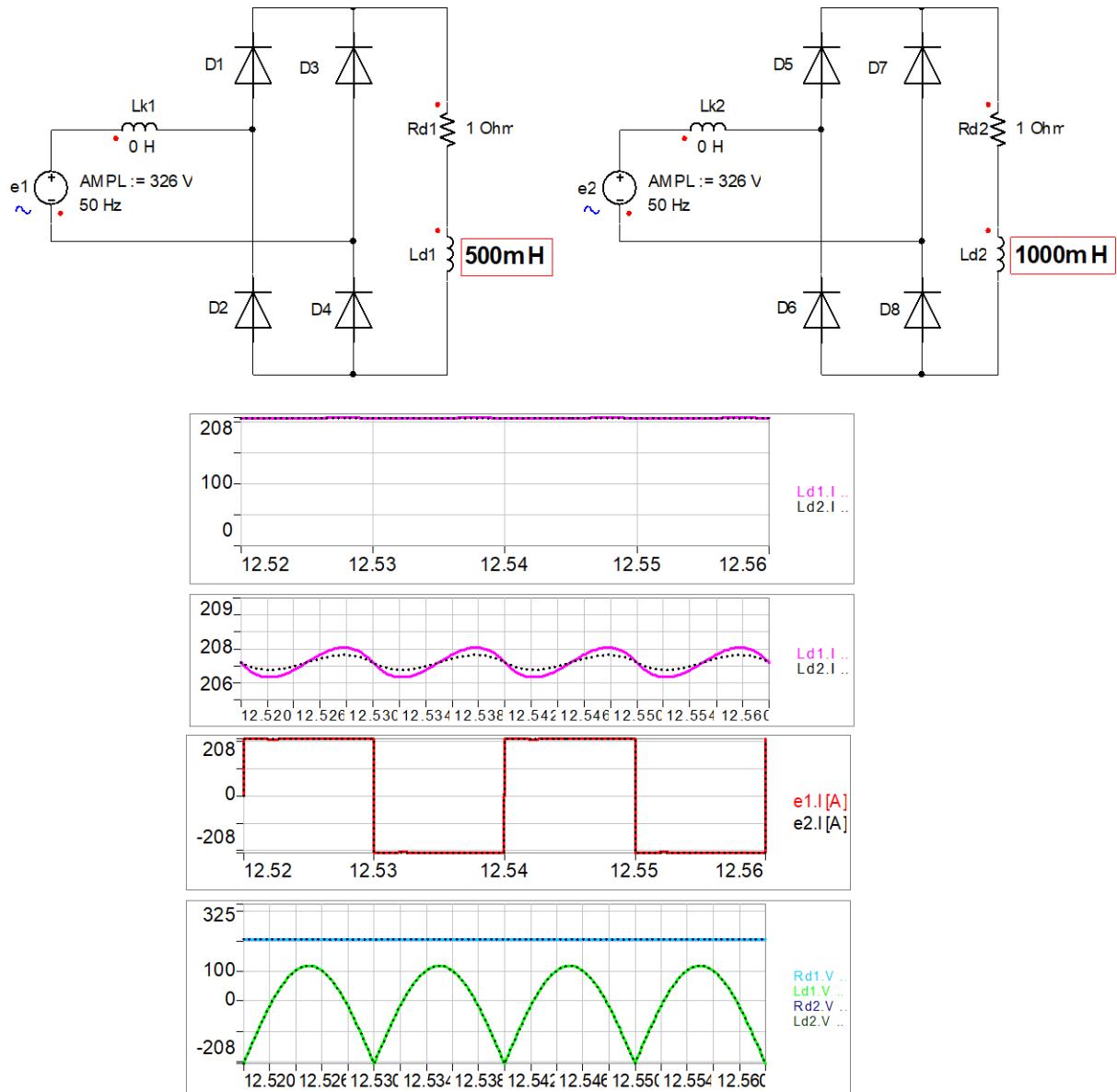
## Dependance of the rectifier waveforms on the load inductance $L_d$



Load inductance does not affect the average load current, but only its ripple.