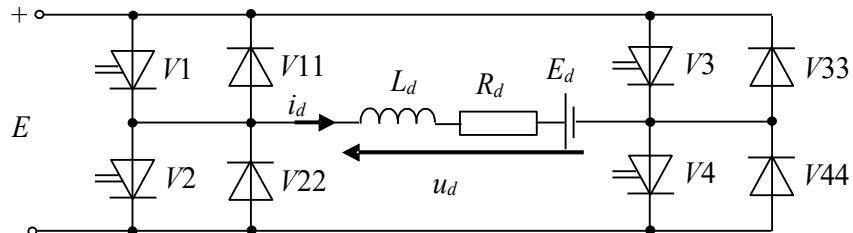



Grupa A

Drugi kolokvij iz Energetske elektronike

1. Odredite napon i struju ventila $V1$ ako se $4/5$ sklopne periode upravljački impuls i stovremeno dovode na ventile $V1$ i $V4$, a $1/5$ sklopne periode istovremeno na ventile $V2$ i $V3$. Zadano je $f_s = 4 \text{ kHz}$, $E = 64 \text{ V}$, $E_d = 10 \text{ V}$, $R_d = 10 \Omega$, $L_d = 50 \text{ mH}$. (2 boda)




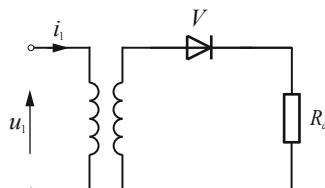2. Odredite valni oblik struje pojne mreže i_1 i radnu snagu trošila $R_d = 20 \Omega$ ako je transformator savršen, prijenosnog omjera $5:1$, zanemarive izmjenične komponente struje magnetiziranja i priključen je na izmjeničnu pojnu mrežu $210\text{V}/50\text{Hz}$. (2 boda)




3. Nacrtajte valni oblik struje pojne mreže kapacitivno opterećenog jednofaznog mosnog spoja. (1 bod)

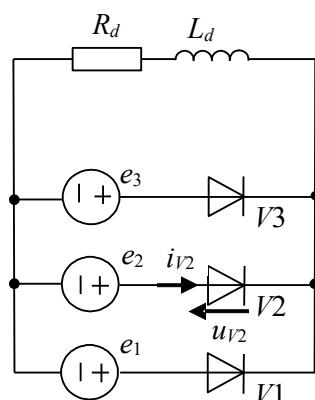4. Za ispravljač s naponima faza $e_1 = 230\sqrt{2}\sin 100\pi t, \text{ V}$, $e_2 = 230\sqrt{2}\sin(100\pi t - 120^\circ), \text{ V}$ i $e_3 = 230\sqrt{2}\sin(100\pi t - 240^\circ), \text{ V}$ opterećen induktivnim trošilom $L_d = 350 \text{ mH}$, $R_d = 5 \Omega$ odredite struju i napon ventila $V2$. (3 boda)



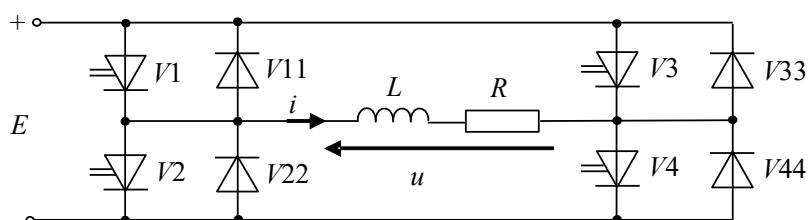
5. Nacrtajte kvalitativno valni oblik struja i_{V4} i i_{V44} fazno upravljanog naponskog izmjenjivača ako je kut upravljanja $\alpha = 60^\circ\text{el}$. (2 boda)




Grupa B

Drugi kolokvij iz Energetske elektronike

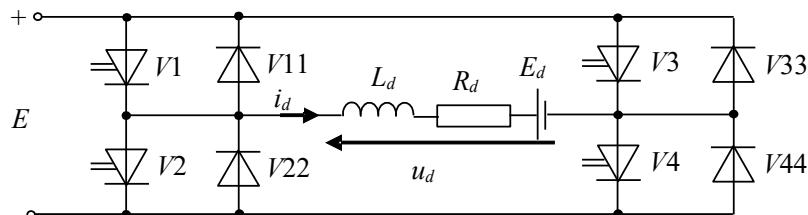1. Odredite struju i napon ventila V_{33} ako se 2/3 sklopne periode upravljački impulsni istovremeno dovode na ventile V_1 i V_4 , a 1/3 sklopne periode istovremeno na ventile V_2 i V_4 . Zadano je $f_s = 12 \text{ kHz}$, $E = 300 \text{ V}$, $E_d = 80 \text{ V}$, $R_d = 20 \Omega$, $L_d = 50 \text{ mH}$. (2 boda)




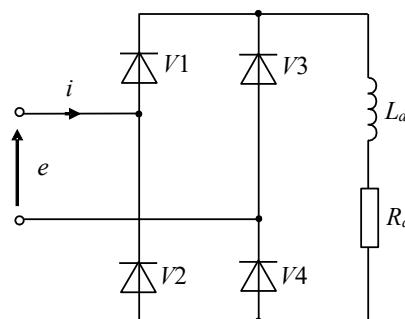2. U krugu na slici odredite valni oblik struje pojne mreže, ako je $e = 320\sin 100\pi t$, V, a trošilo parametara $R_d = 2 \Omega$, $L_d = 180 \text{ mH}$. (2 boda)




3. Nacrtajte valni oblik struja ventila V_2 i V_4 kapacitivno opterećenog jednofaznog mosnog spoja. (2 boda)

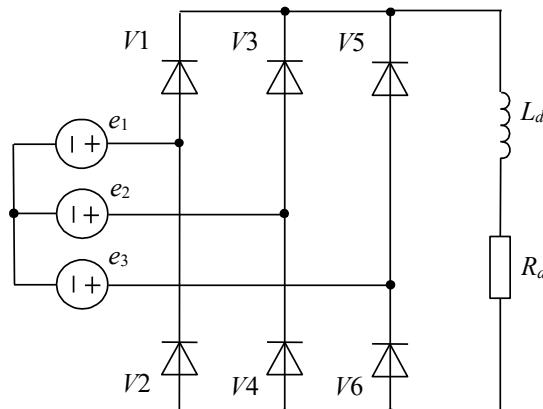4. Za ispravljač s naponima faza $e_1 = 310\sin 100\pi t$, V, $e_2 = 310\sin(100\pi t - 120^\circ)$, V i $e_3 = 310\sin(100\pi t - 240^\circ)$, V opterećen induktivnim trošilom $L_d = 1 \text{ H}$, $R_d = 4 \Omega$ odredite struju i napon ventila V_2 . (2 boda)



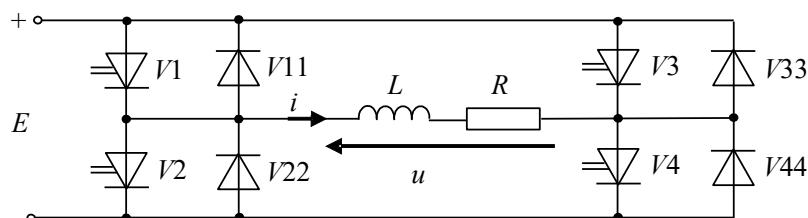5. Nacrtajte kvalitativno valni oblik struja i_{V_1} i $i_{V_{11}}$ i napona u_{V_1} fazno upravljanog naponskog izmjenjivača ako je kut upravljanja $\alpha = 0$. (2 boda)



Djelomična rješenja drugog kolokvija iz Energetske elektronike
održanog 14.06.2018.

Grupa A

1. $I_d(0) = [U_d(0) - E_d]/R_d = 2,84 \text{ A}, \Delta i_d = \alpha T_s/[E - E_d - R_d I_d(0)]/L_d = 102,4 \text{ mA}$

$$0 \leq t \leq 200 \mu\text{s} \quad \dots \quad i_d = 2,7888 + 512t, \text{ A} \quad i_{V1} = i_d \quad u_{V1} = 0$$


$$200 \leq t \leq 250 \mu\text{s} \quad \dots \quad i_d = 3,3008 - 2048t, \text{ A} \quad i_{V1} = 0 \quad u_{V1} = E$$

2. $\hat{I}_d = \hat{U}_s(0)/R_d = 2,9698 \text{ A}, P = 44,1 \text{ W}$

$$0 \leq \omega t \leq \pi \quad \dots \quad i_1 = 594,0 \sin \omega t - 189,1, \text{ mA}$$

$$\pi \leq \omega t \leq 2\pi \quad \dots \quad i_1 = -189,1, \text{ mA}$$

3.

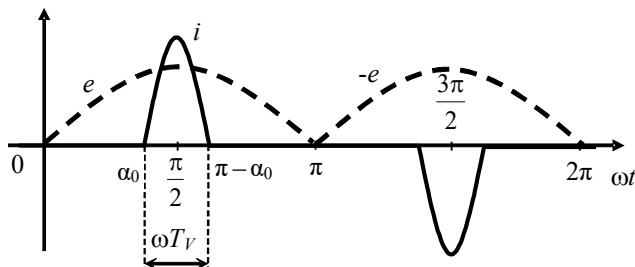

4. $T = 20 \text{ ms}, U_d(0) = 3\sqrt{3}\hat{E}/2\pi = 269,0 \text{ V}, I_d(0) = 53,80 \text{ A}$

$$T/12 \leq t \leq 5T/12 \quad \dots \quad i_{V2} = 0 \quad u_{V2} = e_2 - e_1 = \dots \text{ (vodi } V1)$$

$$5T/12 \leq t \leq 3T/2 \quad \dots \quad i_{V2} = I_d(0) \quad u_{V2} = 0$$

$$3T/2 \leq t \leq 13T/12 \quad \dots \quad i_{V2} = 0 \quad u_{V2} = e_2 - e_3 = \dots \text{ (vodi } V3)$$

5. $i_{V4} = \dots \quad i_{V4} = \dots$

Grupa B

1. $I_d(0) = [U_d(0) - E_d]/R_d = 6 \text{ A}, \Delta i_d = \alpha T_s/[E - E_d - R_d I_d(0)]/L_d = 111,1 \text{ mA}$

$$0 \leq t \leq 55,6 \mu\text{s} \quad \dots \quad i_L = 5,944 + 2000t, \text{ A} \quad i_{V33} = 0 \quad u_{V33} = -E$$


$$55,6 \mu\text{s} \leq t \leq 83,3 \mu\text{s} \quad \dots \quad i_L = 6,278 - 4000t, \text{ A} \quad i_{V33} = 0 \quad u_{V33} = -E$$

2. $T = 20 \text{ ms}, U_d(0) = 2\hat{E}/\pi = 203,72 \text{ V}, I_d(0) = U_d(0)/R_d = 101,86 \text{ A}$

$$0 \leq t \leq T/2 \quad \dots \quad i = I_d(0) = 101,9 \text{ A}$$

$$T/2 \leq t \leq T \quad \dots \quad i = -I_d(0) = -101,9 \text{ A}$$

3.

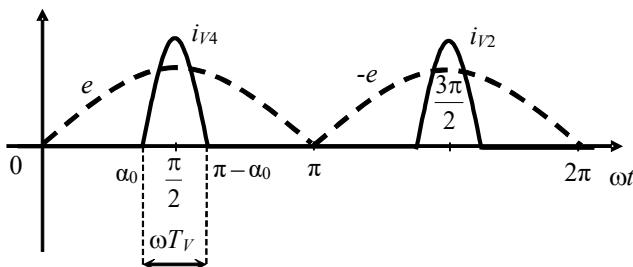

4. $T = 20 \text{ ms}, U_d(0) = 3\sqrt{3}\hat{E}/\pi = 512,7 \text{ V}, I_d(0) = 128,2 \text{ A}$

$$-T/12 \leq t \leq 7T/12 \quad \dots \quad i_{V2} = 0 \quad u_{V2} = u_{A0} - e_1$$

$$7T/12 \leq t \leq 11T/12 \quad \dots \quad i_{V2} = I_d(0) \quad u_{V2} = 0$$

5. $0 \leq t \leq T/2 \quad \dots \quad u_{V1} = 0 \quad i_{V11} = \dots \quad i_{V1} = \dots$

$$T/2 \leq t \leq T \quad \dots \quad u_{V1} = E \quad i_{V11} = \dots \quad i_{V1} = \dots$$

Željko Stojanović

nositelj predmeta