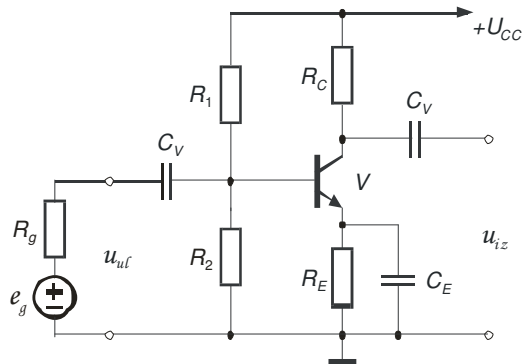


1. domaća zadaća iz Analognih sklopova i Elektroničkih sklopova

1. U krugu na slici napisati jednadžbe SRP-a i DRP-a te odrediti vrijednost otpornika R_2 da se postigne najveći maksimalni hod signala. Poznato je: $U_{CC} = 24 \text{ V}$, $R_1 = 1 \text{ M}\Omega$, $R_C = 6,2 \text{ k}\Omega$, $R_E = 1,1 \text{ k}\Omega$, $\beta = 130$, $U_{BEQ} = 0,7 \text{ V}$, $U_{CEZas} = 0$.

**Rješenje:**

Uvjet za najveći maksimalni hod signala $R_C \cdot I_{CQ} = U_{CEQ} - U_{CEZas}$

Radna točka uvrštena u SRP $U_{CEQ} + (R_C + R_E) \cdot I_{CQ} = U_{CC}$

$$I_{CQ} = \frac{U_{CC}}{2R_C + R_E} = 1,77 \text{ mA}, \quad U_{CEQ} = 11,02 \text{ V} = U_{izmm}$$

$$I_{BQ} = \frac{I_{CQ}}{\beta} = 13,68 \mu\text{A}$$

$$U_B = U_{BEQ} + R_E \cdot I_{CQ} = 2,655 \text{ V}$$

$$I_1 = \frac{U_{CC} - U_B}{R_1} = 21,34 \mu\text{A}, \quad I_2 = I_1 - I_{BQ} = 7,669 \mu\text{A},$$

$$R_2 = \frac{U_B}{I_2} = 346,3 \text{ k}\Omega$$

$$\text{SRP} \dots \boxed{I_C = -\frac{1}{R_C + R_E} \cdot U_{CE} + \frac{U_{CC}}{R_C + R_E} = -137,0 \cdot U_{CE} + 3288 \mu\text{A}}$$

$$\text{DRP} \dots \boxed{i_C = -\frac{1}{R_C} \cdot u_{CE} + \frac{U_{CEQ}}{R_C} + I_{CQ} = -161,3 \cdot u_{CE} + 3556 \mu\text{A}}$$