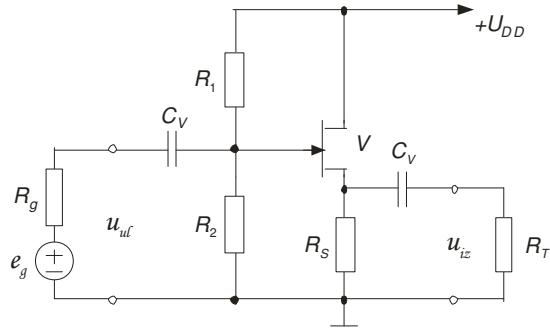


7. domaća zadaća iz Analognih sklopova i Elektroničkih sklopova

1. Na pojačalo sa slike spojen je naponski izvor $e_g = \sin\omega t$, V. Izračunajte izlazni napon pojačala u_{iz} . Poznato je: $U_{DD} = 12$ V, $R_1 = 1$ MΩ, $R_2 = 390$ kΩ, $R_S = 1,5$ kΩ, $U_P = 5$ V, $I_{DSS} = 8$ mA, $\mu = 90$, $R_g = 200$ kΩ, $R_T = 1$ kΩ.

**Rješenje:**

$$U_{GG} = U_{GSQ} + R_S \cdot I_{DQ} \quad (1)$$

$$U_{GG} = \frac{R_2}{R_1 + R_2} \cdot U_{DD} = 3,367 \text{ V}$$

$$I_{DQ} = I_{DSS} \cdot \left(1 + \frac{U_{GSQ}}{U_P} \right)^2 \quad (2) \quad (1) \rightarrow (2)$$

$$I_{DQ} = \frac{U_{GG} - U_{GSQ}}{R_S} = \frac{I_{DSS} \cdot U_{GSQ}^2}{U_P^2} + \frac{2U_{GSQ} \cdot I_{DSS}}{U_P} + I_{DSS}$$

$$U_{GSQ}^2 + U_{GSQ} \cdot \left(2U_P + \frac{U_P^2}{R_S \cdot I_{DSS}} \right) + U_P^2 - \frac{U_{GG} \cdot U_P^2}{R_S \cdot I_{DSS}} = 0$$

$$U_{GSQ}^2 + 12,083U_{GSQ} + 17,986 = 0 \quad U_{GSQ1} = -1,739 \text{ V}, \quad U_{GSQ2} = -10,34 \text{ V}$$

$$U_{GSQ} = -1,739 \text{ V}$$



Drugo se rješenje $U_{GSQ2} = -10,34$ V odbacuje. To bi značilo da FET ne vodi. Uvrštenjem $I_{DQ} = 0$ u izraz (1) ne dobije se da je $U_{GSQ2} = -10,34$ V što je u suprotnosti s polaznom pretpostavkom.

$$I_{DQ} = 3,404 \text{ mA}$$

$$U_{DSQ} = U_{DD} - R_S \cdot I_{DQ} = 6,894 \text{ V}$$

$$g_m = \left. \frac{\partial I_D}{\partial U_{GS}} \right|_{U_{GS}=U_{GSQ}} = \frac{2I_{DSS}}{U_P} \cdot \left(1 + \frac{U_{GSQ}}{U_P} \right) = 2,087 \frac{\text{mA}}{\text{V}}$$
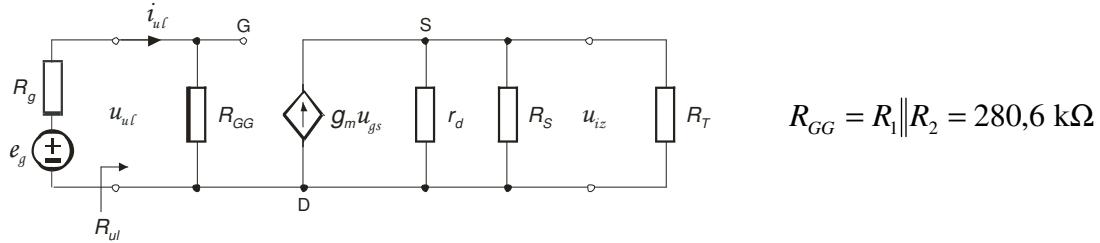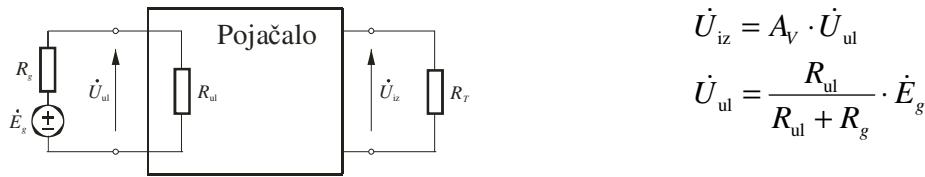
$$r_d = \frac{\mu}{g_m} = 43,12 \text{ k}\Omega$$



$$R_{ul} = \frac{\dot{U}_{ul}}{\dot{I}_{ul}} = R_{GG} = 280,6 \text{ k}\Omega$$

$$A_V = \frac{\dot{U}_{iz}}{\dot{U}_{ul}} = \dots = \frac{u_{iz}}{u_{ul}} = \frac{g_m \cdot u_{gs} \cdot r_d \| R_s \| R_T}{u_{gs} + g_m \cdot u_{gs} \cdot r_d \| R_s \| R_T} = \frac{g_m \cdot r_d \| R_s \| R_T}{1 + g_m \cdot r_d \| R_s \| R_T} = 0,5526$$

$$r_d \| R_s \| R_T = 591,8 \Omega$$

$$\dot{U}_{ul} = \frac{R_{ul}}{R_{ul} + R_g} \cdot \dot{E}_g = 0,5838 \cdot \dot{E}_g$$

$$u_{ul} = 583,8 \sin \omega t, \text{ mV}$$

$$u_{iz} = 322,6 \sin \omega t, \text{ mV}.$$