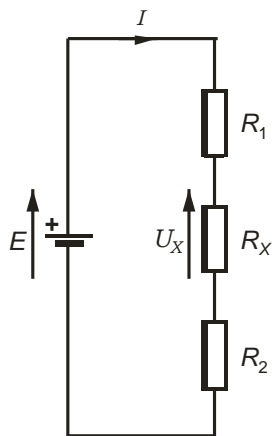



2. domaća zadaća iz Osnova elektrotehnike i elektronike

- U krugu na slici poznato je: $E = 120 \text{ V}$, $R_1 = 30 \Omega$, $R_2 = 60 \Omega$, $U_X = 40 \text{ V}$. Izračunajte I , U_1 , R_X i U_2 .
- U spoju na slici zadano je: $I = 10 \text{ A}$, $I_2 = 2 \text{ A}$, $R_1 = 20 \Omega$, $R_2 = 40 \Omega$. Izračunajte E , R_X i I_X .

1.



2.

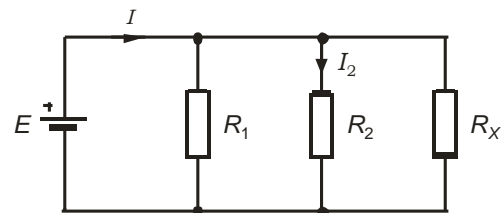

Rješenja

$$1. \quad E = U_1 + U_X + U_2 = R_1 \cdot I_1 + U_X + R_2 \cdot I_2$$

$$I_1 = I_2 = I_X = I$$


$$E = (R_1 + R_2) \cdot I + U_X$$

$$I = \frac{E - U_X}{R_1 + R_2} = \frac{80}{90} = 0,88 \text{ A}$$

$$U_1 = R_1 \cdot I = 26,6 \text{ V}$$

$$U_2 = R_2 \cdot I = 53,3 \text{ V}$$


$$R_X = \frac{U_X}{I} = 45 \Omega$$

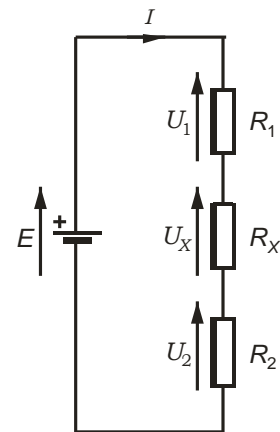

Provjera za napone $U_1 + U_2 = E - U_X \quad \dots \quad 80 = 80$

Provjera za struju $I = \frac{E}{R_1 + R_x + R_2} = \frac{120}{135} = 0,8\bar{8} \text{ A}$

2.

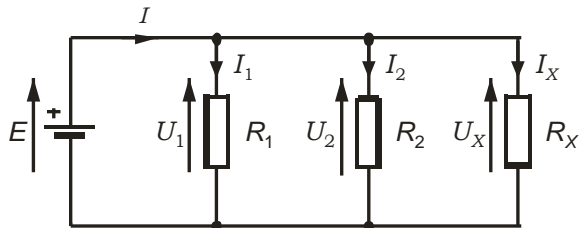

$$I = I_1 + I_2 + I_x$$

$$U_1 = U_2 = U_x = E$$

$$U_2 = R_2 \cdot I_2 = 80 \text{ V}$$

$$E = 80 \text{ V}$$

$$I_1 = \frac{U_1}{R_1} = 4 \text{ A}$$

$$I_x = I - I_1 - I_2 = 4 \text{ A}$$

$$R_x = \frac{U_x}{I_x} = 20 \Omega$$

Provjera

$$E = R_{uk} \cdot I$$

$$R_{uk} = R_1 \parallel R_2 \parallel R_x = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_x}} = 8 \Omega,$$

$$E = 8 \cdot 10 = 80 \text{ V}$$