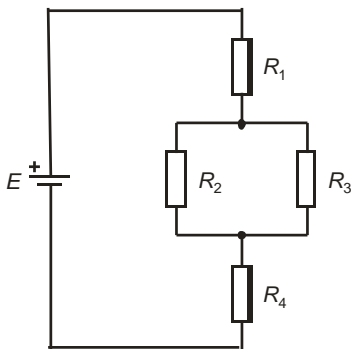



### 3. domaća zadaća iz Osnova elektrotehnike i elektronike

1. Odrediti struje i napone na otpornicima. Zadano je:  $E = 200 \text{ V}$ ,  $R_1 = 50 \text{ } \Omega$ ,  $R_2 = 30 \text{ } \Omega$ ,  $R_3 = 60 \text{ } \Omega$ ,  $R_4 = 30 \text{ } \Omega$ .
2. U spoju na slici zadano je:  $R_1 = 10 \text{ } \Omega$ ,  $R_2 = 20 \text{ } \Omega$ ,  $R_3 = 30 \text{ } \Omega$ ,  $R_4 = 12 \text{ } \Omega$ ,  $I_3 = 2 \text{ A}$ . Izračunajte  $E$ ,  $I_1$ ,  $I_2$  i  $I_4$ .
3. U dijelu mreže prikazanom na slici poznato je:  $R_2 = R_3 = 5 \text{ } \Omega$ ,  $I_A = 12 \text{ A}$ ,  $I_B = 4 \text{ A}$ ,  $I_1 = 2 \text{ A}$ . Izračunajte  $I_C$ ,  $I_2$ ,  $I_3$  i  $R_1$ .


1.



2.

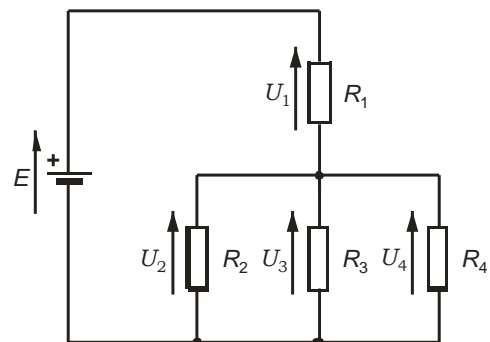

3.

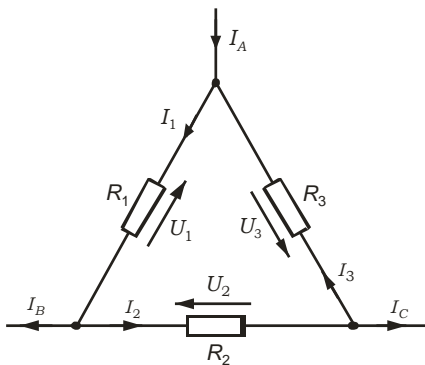


### Rješenja

$$1. \quad R_{23} = \frac{R_2 \cdot R_3}{R_2 + R_3} = 20 \text{ } \Omega$$

$$R_{uk} = R_1 + R_{23} + R_4 = 100 \text{ } \Omega$$

$$I = \frac{E}{R_{uk}} = 2 \text{ A}$$

$$I_1 = I_4 = I_{23} = I$$

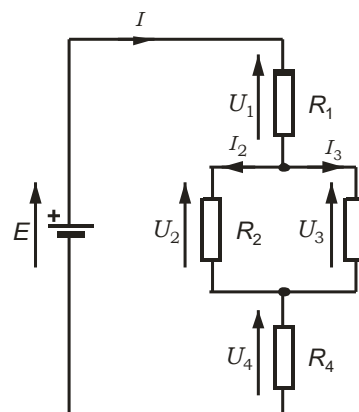

$$U_1 = R_1 \cdot I_1 = 100 \text{ V}$$

$$U_2 = U_3 = U_{23} = R_{23} \cdot I_{23} = 40 \text{ V}$$

$$I_2 = \frac{U_2}{R_2} = 1,33 \text{ A}$$

$$I_3 = \frac{U_3}{R_3} = 0,66 \text{ A}$$

$$U_4 = R_4 \cdot I_4 = 60 \text{ V}$$

Provjera za struje  $I_1 = I_2 + I_3 \quad \dots \quad 2 = 1,33 + 0,66$

Provjera za napone  $E = U_1 + U_2 + U_4 \quad \dots \quad 200 = 100 + 40 + 60$

2.  $U_3 = R_3 \cdot I_3 = 60 \text{ V}$

$$U_2 = U_4 = U_3$$

$$I_2 = \frac{U_2}{R_2} = 3 \text{ A}$$

$$I_4 = \frac{U_4}{R_4} = 5 \text{ A}$$

$$I_1 = I_2 + I_3 + I_4 = 10 \text{ A}$$

$$U_1 = R_1 \cdot I_1 = 100 \text{ V}$$

$$E = U_1 + U_2 = 160 \text{ V}$$

Provjera


$$R_{234} = R_2 \parallel R_3 \parallel R_4 = \frac{1}{\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}} = 6 \Omega$$

$$R_{uk} = R_1 + R_{234} = 16 \Omega$$

$$I_1 = \frac{E}{R_{uk}} = 10 \text{ A}$$

$$\left. \begin{array}{l} \frac{U_1}{R_1} = \frac{U_{234}}{R_{234}} \\ U = U_1 + U_{234} \end{array} \right\}$$
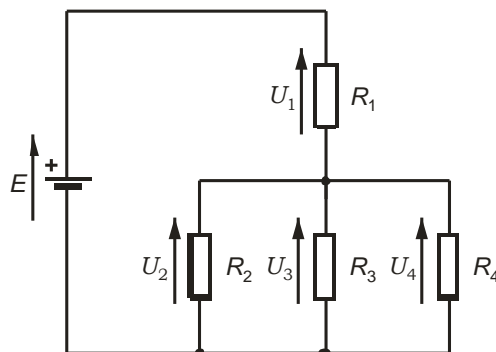
$$U_{234} = \frac{R_{234}}{R_1 + R_{234}} \cdot E = \frac{6}{16} \cdot 160 = 60 \text{ V}$$



3.  $I_3 = I_1 - I_A = -10 \text{ A}$

$$U_3 = R_3 \cdot I_3 = -50 \text{ V}$$

$$I_A = I_B + I_C$$

Cijeli trokut s otpornicima  $R_1$ ,  $R_2$ ,  $R_3$  ponaša se kao čvor u kojeg ulaze ili iz njega izlaze struje  $I_A$ ,  $I_B$ ,  $I_C$ .


$$I_C = I_A - I_B = 8 \text{ A}$$

$$I_2 = I_C + I_3 = -2 \text{ A}$$

$$U_2 = R_2 \cdot I_2 = -10 \text{ V}$$

$$U_1 = -U_2 - U_3 = 60 \text{ V}$$
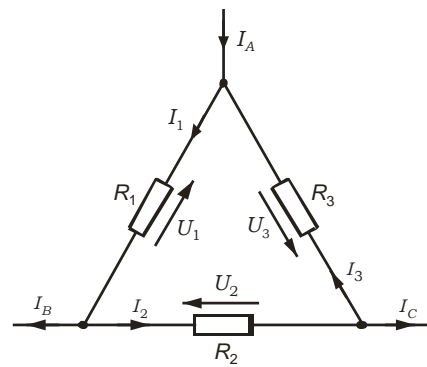
$$R_1 = \frac{U_1}{I_1} = 30 \text{ } \Omega$$



Provjera

$$I_1 = I_2 + I_B = -2 + 4 = 2 \text{ A}$$