

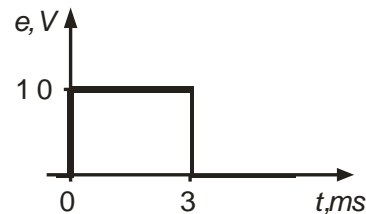


4. domaća zadaća iz Osnova elektrotehnike i elektronike

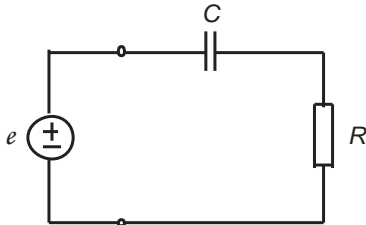1. Ulazni napon kao sa slike priključen je na RC -spoj. Napišite izraze za napon na otporniku u intervalima od 0 do 3 ms i od 3 ms do ∞ te ga nacrtajte. Poznato je: $R = 47 \text{ k}\Omega$, $C = 33 \text{ nF}$.




Rješenje:

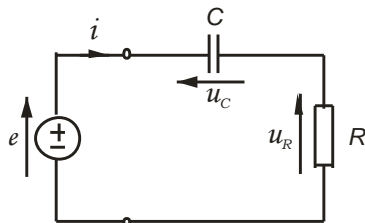

$$e = u_C + u_R$$
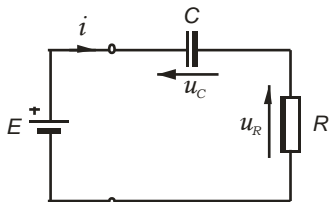
$$\underline{0 \leq t \leq 3 \text{ ms}}$$




$$e = 10 \text{ V} = E, \quad \tau = RC = 1,551 \text{ ms}$$

$$u_C = E \cdot \left(1 - e^{-\frac{t}{\tau}}\right) = 10 \cdot \left(1 - e^{-\frac{t}{1,551 \cdot 10^{-3}}}\right)$$

$$u_R = E \cdot e^{-\frac{t}{\tau}} = 10 \cdot e^{-\frac{t}{1,551 \cdot 10^{-3}}}$$

$$u_C(3 \text{ ms}) = 10 \cdot \left(1 - e^{-\frac{3}{1,551}}\right) = 10 \cdot (1 - 0,1445) = 8,555 \text{ V}$$

$$\underline{t > 3 \text{ ms}}$$

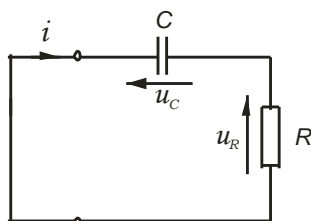

$$0 = u_C + u_R, \quad \tau = RC = 1,551 \text{ ms}$$

$$u_C = u_C(t = 3 \text{ ms}) \cdot e^{-\frac{t-3 \cdot 10^{-3}}{\tau}} = 8,555 \cdot e^{-\frac{t-3 \cdot 10^{-3}}{1,551 \cdot 10^{-3}}}$$

$$u_R = -u_C$$

$$u_R = -8,555 \cdot e^{-\frac{t-3 \cdot 10^{-3}}{1,551 \cdot 10^{-3}}}$$

Prikaz napona u krugu.

